

---

# MOSFET Switches

---

**Ghassan Arnouk**  
**Samuel (Wendi) Zhu**

ELEC 3500B  
Winter 2020  
Lab 1 Report

**Instructor:** Ralph Mason  
**Date Performed:** January 22, 2020

**Date Submitted:** January 23, 2020

## Table of Contents

List of Tables .....	3
List of Figures .....	3
1.2 NMOS Transistor .....	4
Q1: Simulate the circuit in Figure 2.2 to find the lowest output voltage $V_{out}$ (min) with different values of R. (Try $R=10\text{ k}\Omega$ , $R=25\text{ k}\Omega$ , $50\text{ k}\Omega$ , $200\text{ k}\Omega$ , $1000\text{ k}\Omega$ ).....	4
Q2.....	6
Q3: With $R = 200\text{ k}\Omega$ , $L = 1\mu\text{m}$ , sweep W (the width of the transistor) from $1\mu\text{m}$ to $10\mu\text{m}$ (at least 4 points), and for each value measure the delay from $V_{in}$ rising to $1.25\text{V} \rightarrow V_{out}$ falling to $1.25\text{V}$ . <i>Plot the simulation sweep</i> , and plot the measurement results for your report. ....	7
Q4: Keep $R = 200\text{ k}\Omega$ , $W = 1\mu\text{m}$ , sweep L (the length of the transistor) from $1\mu\text{m}$ to $10\mu\text{m}$ (at least 4 points), and for each value measure the delay from $V_{in}$ rising to $1.25\text{V} \rightarrow V_{out}$ falling to $1.25\text{V}$ . <i>Plot the simulation sweep</i> , and plot the measurement results for your report. ....	9
Q5: Run simulations of the circuit in Figure 2.4 for different values of R, and .....	10
Q6: Comment: Would you think digital circuits would perform better when NMOS transistors were connected to pull the output up or down? .....	11
1.3 PMOS Transistor .....	12
Q7: Simulate the circuit in Figure 2.5 to find $V_{out}$ for a range of R.....	12
Q8: Simulate the circuit in Figure 2.6 to plot $V_{out\text{ max}}$ Vs. R, particularly find the maximum $V_{out}$ .....	13
Q9: Comment: Would you think digital circuits would perform better when PMOS transistors were connected to pull the output up or down? .....	15
Q10.....	15

## List of Tables

Table 1 - Minimum $V_{out}$ VS. R .....	4
Table 2 - Collected Data Using Cursors for Delay Time Vs. W.....	8
Table 3 - Collected Data Using Cursors for Delay Time Vs. L.....	9
Table 4 - $V_{out}$ Max Vs. R.....	11
Table 5 - $V_{out}$ min Vs. R.....	12
Table 6 - $V_{out}$ min Vs. R.....	14

## List of Figures

Figure 1 - Plot of $V_{out}$ Vs. R = 10 k $\Omega$ , 25 k $\Omega$ , 50 k $\Omega$ , 200 k $\Omega$ , 1000 k $\Omega$ .....	4
Figure 2 - Plot of min $V_{out}$ Vs. R for NMOS Transistor Pulling Down .....	5
Figure 3 - Plot for Delay Time from $V_{in}$ rising to 1.25V to $V_{out}$ falling to 1.25V with R = 200 k $\Omega$ .....	5
Figure 4 - Plot for $V_{in}$ and $V_{out}$ for R = 1000 k $\Omega$ .....	6
Figure 5 - Simulation Plot of $I_d$ Vs. $V_{GS}$ .....	6
Figure 6 – Simulation Sweep of W from 1 $\mu$ m to 10 $\mu$ m with R = 200 k $\Omega$ and L = 1 $\mu$ m .....	7
Figure 7 - Plot of Delayed Time Vs. W .....	8
Figure 8 – Simulation Sweep for L from 1 $\mu$ m to 10 $\mu$ m with R = 200k $\Omega$ and W = 1 $\mu$ m .....	9
Figure 9 – Plot of delay Time Vs. L .....	10
Figure 10 - Simulation of the Circuit in Fig. 2.4 for R =10k $\Omega$ , 25k $\Omega$ , 50k $\Omega$ , 200k $\Omega$ , and 1000k $\Omega$ .....	10
Figure 11 - Plot of $V_{out}$ Max Vs. R .....	11
Figure 12 - The Simulation Plot of $V_{out}$ for R =10k $\Omega$ , 25k $\Omega$ , 50k $\Omega$ , 200k $\Omega$ , 1000k $\Omega$ .....	12
Figure 13 - $V_{out}$ min Vs. R for Pulling Down with a PMOS .....	13
Figure 14 - Simulation Plot for $V_{out}$ Vs. R for R =10k $\Omega$ , 25k $\Omega$ , 50k $\Omega$ , 200k $\Omega$ , 1000k $\Omega$ . .....	14
Figure 15 - $V_{out}$ Max Vs. R for PMOS Transistor Pulling Up .....	14
Figure 16 - The Simulation Plot for $V_{in}$ and $V_{out}$ with R = 200 k $\Omega$ .....	15
Figure 17 - Zoomed-in Plot to Calculated the Delay Time.....	16

## 1.2 NMOS Transistor

### 1.2.1 Transistor Pulling Down

Q1: Simulate the circuit in Figure 2.2 to find the lowest output voltage  $V_{out}$  (min) with different values of R. (Try  $R=10\text{ k}\Omega$ ,  $R=25\text{ k}\Omega$ ,  $50\text{ k}\Omega$ ,  $200\text{ k}\Omega$ ,  $1000\text{ k}\Omega$ )

a) Figure 1 below shows the plot of  $V_{out}$  Vs. R for different values of R.

 


Figure 1 - Plot of  $V_{out}$  Vs.  $R = 10\text{ k}\Omega$ ,  $25\text{ k}\Omega$ ,  $50\text{ k}\Omega$ ,  $200\text{ k}\Omega$ ,  $1000\text{ k}\Omega$ .

Table 1 - Minimum  $V_{out}$  VS.  $R$

R (kΩ)	10	25	50	200	1000
$V_{out}$ min (mV)	754	317	160.5	40.4	8.1

Table 1 above shows the minimum  $V_{out}$  data collected using the cursor for  $R = 10\text{ k}\Omega$ ,  $25\text{ k}\Omega$ ,  $50\text{ k}\Omega$ ,  $200\text{ k}\Omega$ ,  $1000\text{ k}\Omega$ .

Figure 2 below shows the plot of min  $V_{out}$  Vs. R. The min  $V_{out}$  decreases as R increases, and  $V_{out}$  min was close to 0 for a large value of R. This indicates that the NMOS transistor was good at pulling down the output voltage.

 


Figure 2 - Plot of min  $V_{out}$  Vs.  $R$  for NMOS Transistor Pulling Down

b) What is the delay from  $V_{in}$  rising to 1.25V to  $V_{out}$  falling to 1.25V with  $R = 200 \text{ k}\Omega$

Figure 3 below shows the simulation results to find the delay time from  $V_{in}$  rising to 1.25V to  $V_{out}$  falling to 1.25V with  $R = 200 \text{ k}\Omega$ . Note that the delay time was obtained using the cursor values shown at the bottom right of the screen. Delay time = 434.069 ps.

 


Figure 3 - Plot for Delay Time from  $V_{in}$  rising to 1.25V to  $V_{out}$  falling to 1.25V with  $R = 200 \text{ k}\Omega$

- c) Considering how fast the output would take to charge and discharge (which is normally very important in digital circuits), what is the disadvantage of making  $R$  very high (eg.  $1000\text{ k}\Omega$ )?

Figure 4 below shows the simulation results for  $R = 1000\text{ k}\Omega$ .

 


Figure 4 - Plot for  $V_{in}$  and  $V_{out}$  for  $R = 1000\text{ k}\Omega$

The time for output to charge and discharge will be increased as  $R$  increases because the RC time constant,  $\tau$ , increased. This would limit the time needed for the output voltage to fully charge for high frequency input. The disadvantage of making  $R$  very high is the circuit would not respond quick enough for high frequency input.

Q2

- a) With  $R = 1\text{ k}\Omega$ , using simulations plot  $I_d$  versus  $V_{GS}$

Figure 5 below shows the simulation plot of  $I_d$  Vs.  $V_{GS}$  with  $R = 1\text{ k}\Omega$ .

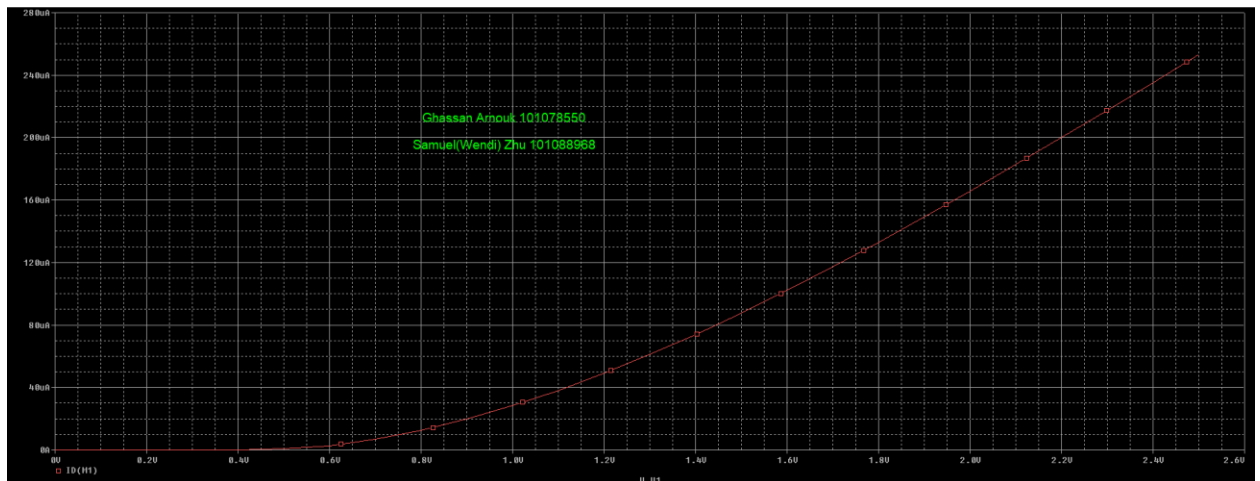


Figure 5 - Simulation Plot of  $I_d$  Vs.  $V_{GS}$

- b) Is there a sharply defined threshold voltage, above which the transistor starts conducting?

The transistor starts conducting at roughly 0.43V which is the threshold voltage.

- c) From your plot, make an estimate for this value. Find corresponding current and compare it to the maximum current.

The threshold voltage is approximately 0.43 V since the transistor starts conducting with current  $I_d = 2.75\text{nA}$ . The maximum current, taken from the plot, is 253uA, which occurred at 2.5V. The corresponding current of when the transistor starts conducting was very small in comparison to the maximum current.

Q3: With  $R = 200\text{ k}\Omega$ ,  $L = 1\mu\text{m}$ , sweep  $W$  (the width of the transistor) from  $1\mu\text{m}$  to  $10\mu\text{m}$  (at least 4 points), and for each value measure the delay from  $V_{in}$  rising to  $1.25 \rightarrow V_{out}$  falling to 1.25. Plot the simulation sweep, and plot the measurement results for you report.

Figure 6 below shows the simulation sweep plot of  $W$  from  $1\mu\text{m}$  to  $10\mu\text{m}$  with  $R = 200\text{ k}\Omega$  and  $L = 1\mu\text{m}$ .

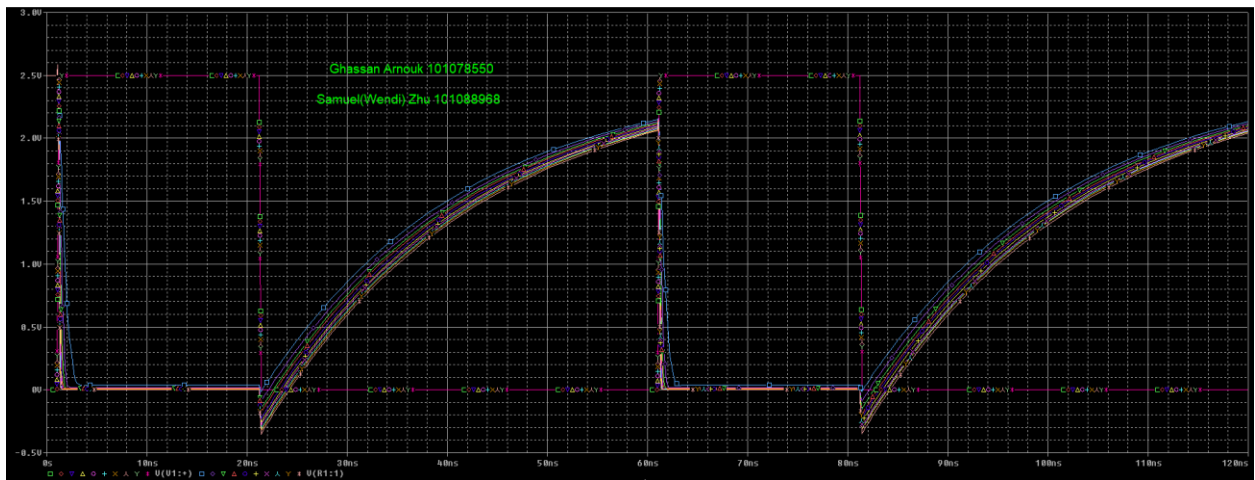



Figure 6 – Simulation Sweep of  $W$  from  $1\mu\text{m}$  to  $10\mu\text{m}$  with  $R = 200\text{ k}\Omega$  and  $L = 1\mu\text{m}$

Table 2 below summarizes the collected data using cursors for delay time versus W.

*Table 2 - Collected Data Using Cursors for Delay Time Vs. W*

W (um)	1	2	4	6	8	10
Delay time (ps)	434	237	142	112.66	98.32	87.12

Figure 7 below shows the plot for delay time Vs. W. The delay time decreases as the width of the transistor increases.

 

*Figure 7 - Plot of Delayed Time Vs. W*



Q4: Keep  $R = 200 \text{ k}\Omega$ ,  $W = 1 \mu\text{m}$ , sweep  $L$  (the length of the transistor) from  $1 \mu\text{m}$  to  $10 \mu\text{m}$  (at least 4 points), and for each value measure the delay from  $V_{\text{in}}$  rising to  $1.25\text{V} \rightarrow V_{\text{out}}$  falling to  $1.25\text{V}$ . *Plot the simulation sweep, and plot the measurement results for your report.*

Figure 8 below shows the simulation sweep plot for  $L$  from  $1 \mu\text{m}$  to  $10 \mu\text{m}$  with  $R = 200 \text{ k}\Omega$  and  $W = 1 \mu\text{m}$ .

 


Figure 8 – Simulation Sweep for  $L$  from  $1 \mu\text{m}$  to  $10 \mu\text{m}$  with  $R = 200 \text{ k}\Omega$  and  $W = 1 \mu\text{m}$

Table 3 summarizes the collected data using the cursors for delay time Vs.  $L$ .

Table 3 - Collected Data Using Cursors for Delay Time Vs.  $L$ .

<b>L (um)</b>	1	2	4	6	8	10
<b>Delay time (ps)</b>	437	771	1544	2400	3484	4400

Figure 9 below shows the plot of delay time Vs. L. They delay time increases as the length of the transistor increases.

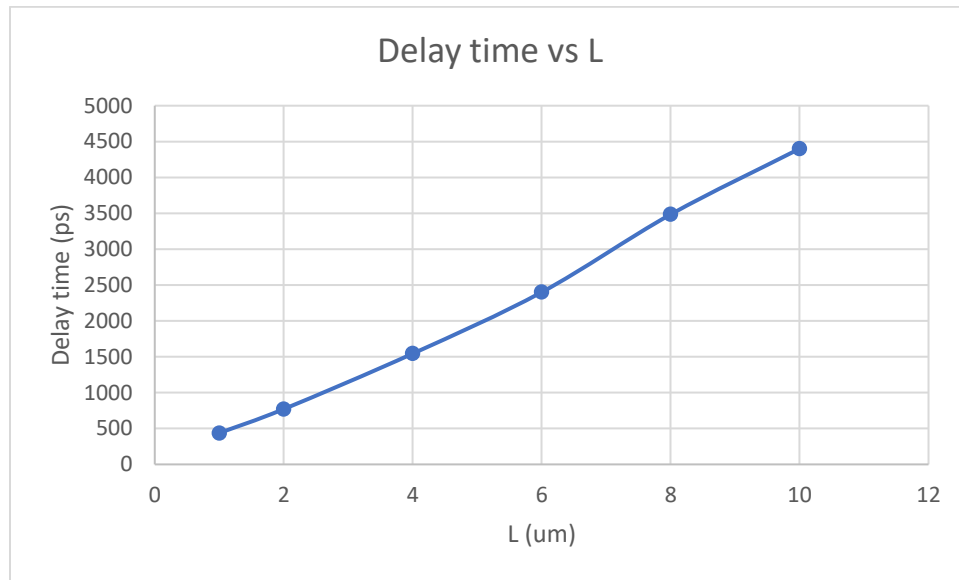


Figure 9 – Plot of delay Time Vs. L

### 1.2.2 Transistor at Top end ( $V_{DD}$ End) of Circuit.

Q5: Run simulations of the circuit in Figure 2.4 for different values of R, and

- a) Find the maximum value of the output voltage(s), plotting them on a curve of  $V_{out}(MAX)$  Vs. R

Figure 10 below shows the simulation results for R = 10k $\Omega$ , 25k $\Omega$ , 50k $\Omega$ , 200k $\Omega$ , and 1000k $\Omega$ .

 



Figure 10 - Simulation of the Circuit in Fig. 2.4 for R =10k $\Omega$ , 25k $\Omega$ , 50k $\Omega$ , 200k $\Omega$ , and 1000k $\Omega$

Table 4 below shows the collected data using cursors for  $V_{out\ max}$  Vs.  $R$ .

*Table 4 -  $V_{out\ Max}$  Vs.  $R$*

<b>R (k<math>\Omega</math>)</b>	10	25	50	200	1000
<b><math>V_{out\ max}</math> (mV)</b>	856	1132.5	1300	1527	1665

Figure 11 shows the plot of  $V_{out\ max}$  Vs.  $R$

 

*Figure 11 - Plot of  $V_{out\ Max}$  Vs.  $R$*

- b) From this plot, what do you estimate the threshold voltage of the NMOS to be? Compare with Q2c.**

The threshold voltage was estimated as followed:

$$V_{TH} \approx 2.5 - 1.7 = 0.8\ V$$

From Q2c, the threshold voltage was estimated as 0.43V. The  $V_{TH}$  estimated here is larger than the threshold voltage estimated from Q2c.

**Q6: Comment: Would you think digital circuits would perform better when NMOS transistors were connected to pull the output up or down?**

The digital circuits would perform better when NMOS transistors were connected to pull the output down.

Using Figure 11 above, the highest  $V_{out}$  that the NMOS transistor could pull up was roughly 1.7V, which was not very close to the supply voltage 2.5V. Using Figure 2 above, the minimum  $V_{out}$  that the NMOS transistor could pull down was very close to 0V. Therefore, digital circuits would perform better when NMOS transistors were connected to pull the output down.

## 1.3 PMOS Transistor

### 1.3.1 Transistor Pulling Down

**Q7: Simulate the circuit in Figure 2.5 to find  $V_{out}$  for a range of R**

Figure 12 below shows the simulation plot of  $V_{out}$  for  $R = 10k\Omega, 25k\Omega, 50k\Omega, 200k\Omega, 1000k\Omega$ .

 


Figure 12 - The Simulation Plot of  $V_{out}$  for  $R = 10k\Omega, 25k\Omega, 50k\Omega, 200k\Omega, 1000k\Omega$ .


a) Plot the graph  $V_{out \text{ min}}$  versus  $R$ .

Table 5 shows the data obtained using the cursors for  $V_{out \text{ min}}$  Vs.  $R$ .

Table 5 -  $V_{out \text{ min}}$  Vs.  $R$

$R \text{ (k}\Omega\text{)}$	10	25	50	200	1000
$V_{out \text{ min}} \text{ (V)}$	2.1232	1.879	1.6847	1.3587	1.1309

Figure 13 below shows the graph of  $V_{out\ min}$  Vs.  $R$ .

 

*Figure 13 -  $V_{out\ min}$  Vs.  $R$  for Pulling Down with a PMOS*

**b) How close can  $V_{out}$  get to 0V?**

The minimum of  $V_{out}$  could go down to roughly 1V. This value was not close to 0.

**c) Estimate the threshold voltage of the PMOS transistor from this.**

The threshold voltage was estimated from Figure 13.0 as followed:

$$|V_{TH}| \approx 1V$$

### 1.3.2 PMOS Transistor Pulling Down

**Q8: Simulate the circuit in Figure 2.6 to plot  $V_{out\ max}$  Vs.  $R$ , particularly find the maximum  $V_{out}$**

Figure 14 below shows the simulation results of the circuit of Fig. 2.6 for  $V_{out}$  versus  $R = 10k\Omega$ ,  $25k\Omega$ ,  $50k\Omega$ ,  $200k\Omega$ ,  $1000k\Omega$ .

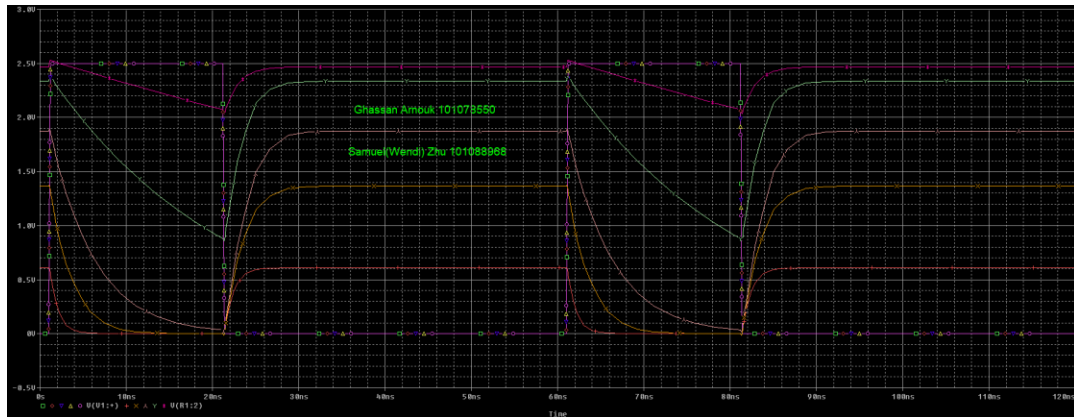


Figure 14 - Simulation Plot for  $V_{out}$  Vs.  $R$  for  $R = 10k\Omega, 25k\Omega, 50k\Omega, 200k\Omega, 1000k\Omega$ .

Table 6 below summarizes measured data using cursors for  $V_{out}$  max Vs.  $R$ .

Table 6 -  $V_{out}$  min Vs.  $R$

$R$ ( $k\Omega$ )	10	25	50	200	1000
$V_{out}$ max (V)	0.609	1.3653	1.8739	2.3343	2.4664

The maximum  $V_{out}$  from the measured data was 2.4664V, which is very close to the supply voltage 2.5V.

Figure 15 below shows the plot of  $V_{out}$  max Vs.  $R$ .

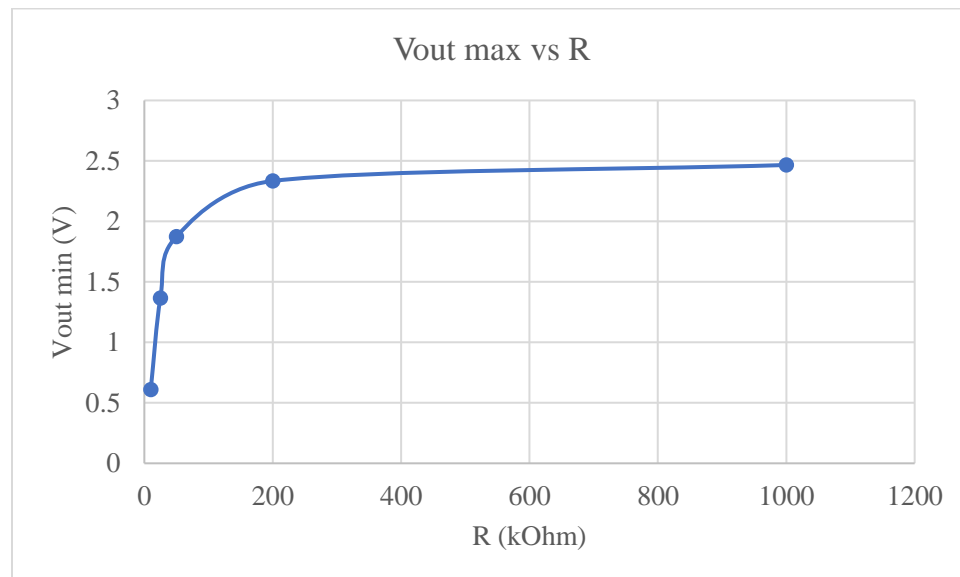


Figure 15 -  $V_{out}$  Max Vs.  $R$  for PMOS Transistor Pulling Up

Q9: Comment: Would you think digital circuits would perform better when PMOS transistors were connected to pull the output up or down?

Digital circuits would perform better when PMOS transistors were connected to pull the output up.

When pulling down with a PMOS transistor (as shown in section 1.3.1), the lowest  $V_{out}$  is roughly 1V due to the threshold voltage, and  $V_{out}$  is not close to 0. When pulling up with a PMOS transistor, the highest  $V_{out}$  is roughly 2.5V, which is close to the supply voltage. Therefore, PMOS transistors were better to connected to pull the output up.

Q10

- a) For  $R = 200\text{ k}\Omega$ , calculate the delay from  $V_{in}$  falling to 1.25V  $\rightarrow$   $V_{out}$  rising to 1.25V. Include this plot in your report.

Figure 16 below shows the simulation plot of  $V_{in}$  and  $V_{out}$  with  $R = 200\text{ k}\Omega$ .

 


Figure 16 - The Simulation Plot for  $V_{in}$  and  $V_{out}$  with  $R = 200\text{ k}\Omega$

Figure 17 below shows the zoomed-in plot to calculate the delay time from  $V_{in}$  falling to 1.25V to  $V_{out}$  rising to 1.25V. Note that the cursors values are shown in the bottom right corner of the plot.

 


Figure 17 - Zoomed-in Plot to Calculated the Delay Time

The time for the first cursor was  $t_1 = 22.129 \text{ ns}$ .

The time for the second cursor was  $t_2 = 21.3 \text{ ns}$ .

Time delay was calculated as:  $\text{Time delay} = t_1 - t_2 = 829.113 \text{ ps}$ .

#### b) How does this compare to the delay of the NMOS? (Refer to Q1)

The delay time for PMOS was around 829 ps, and the delay time for NMOS was around 434 ps. Therefore, the delay time for PMOS is larger than the delay time for NMOS.