

Numbering Systems

Introduction

Verilog HDL modeling language allows numbers being represented in several radix systems. The underlying circuit processes the number in binary, however, input into and output from such circuits is typically done using decimal numbers. In this lab you will learn various representations and methods for converting numbers from one representation into another. Please refer to the Vivado tutorial on how to use the Vivado tool for creating projects and verifying digital circuits.

Objectives

After completing this lab, you will be able to:

- Define a number in various radix
- Design combinatorial circuits capable of converting data represented in one radix into another
- Design combinatorial circuits to perform simple addition operation
- Learn a technique to improve addition speed

Number Representations

Part 1

In Verilog HDL a signal can have the following four basic values:

- 0 : logic-0 or false
- 1 : logic-1 or true
- x : unknown
- z : high-impedance (tri-state)

A z value at the input of a gate or in expression is usually interpreted as an x. In general, Verilog HDL is case-sensitive, but when the values are represented they are case-insensitive.

There are three types of constants in Verilog HDL: (i) integer, (ii) real, and (iii) string. An underscore character (_) can be used in an integer or real constant to improve readability. It cannot appear as the first or last character.

Integer numbers can be written in (i) simple decimal or (ii) base format. An integer in simple decimal form is specified as a sequence of digits with an optional + or a -. For example,

15
-32

where 15 can be represented in binary as 01111 in 5-bit format and -32 can be represented in binary as 100000 in 6-bit format. The simple format representation may result in 32-bit hardware.

A number can be represented in the base format with syntax:

[size] 'base value

where the size specifies the number of bits, base is one of o or O (for octal), b or B (for binary), d or D (for decimal), h or H (for hexadecimal), and value is a sequence of digits which are valid for the specified base. The value must be unsigned. For example,

wire [4:0] 5'O37	5-bit octal representation
reg [3:0] 4'B1x_01	4-bit binary
wire [3:0] 4'd-4	illegal, value cannot be negative
wire [11:0] 7'Hx	7-bit x extended to xxxxxxx

If the size specified is larger than the value for the specified constant, the number is padded to the left with 0's except for the case where the left most bit is x or z then the padding is done with x or z. If the size specified is smaller than the extra leftmost bits are ignored. If the size is not specified then it will use 32-bit data.

Binary Codes

Part 2


Although most processors compute data in binary form, the input-output is generally done in some coded form. Normally, we exchange information in decimal. Hence decimal numbers must be coded in terms of binary representations. In the simplest form of binary code, each decimal digit is replaced by its binary equivalent. This representation is called Binary Coded Decimal (BCD) or 8-4-2-1 (to indicate weight of each bit position). Because there are only ten decimal digits, 1010 through 1111 are not valid BCD. Table below shows some of the widely used binary codes for decimal digits. These codes are designed and used for communication reliability and error detection.

Decimal Digits	BCD (8-4-2-1)	6-3-1-1	Excess-3	2-out-of-5	Gray code
0	0000	0000	0011	00011	0000
1	0001	0001	0100	00101	0001
2	0010	0011	0101	00110	0011
3	0011	0100	0110	01001	0010
4	0100	0101	0111	01010	0110
5	0101	0111	1000	01100	1110
6	0110	1000	1001	10001	1010
7	0111	1001	1010	10010	1011
8	1000	1011	1011	10100	1001
9	1001	1100	1100	11000	1000

2-1. Output 4-bit binary input onto one LED (most significant bit) and the right most 7-segment display (least significant digit) after converting them into two-digit decimal equivalent (BCD). Use only dataflow modeling.

Design a circuit that converts a 4-bit binary number into its 2-digit decimal equivalent, z and m. Since valid input range is between 0 and 15, the most significant digit can be displayed using one LED. The table below shows the required output values. A block diagram of the design is given in the figure below. It includes a comparator that checks when the value of v is greater than 9, and uses the output of this comparator in the control of the 7-segment displays. Hint: The m3 would be zero whenever V is greater than binary 1001.

v[3:0]	z	m[3:0]
0000	0	0000
0001	0	0001
0010	0	0010
0011	0	0011
0100	0	0100
0101	0	0101
0110	0	0110
0111	0	0111
1000	0	1000
1001	0	1001
1010	1	0000
1011	1	0001
1100	1	0010
1101	1	0011
1110	1	0100
1111	1	0101

 

2-1-1. Open Vivado and create a blank project called lab2_2_1.


2-1-2. Create and add the Verilog module (name it as lab2_2_1_partA) with v[3:0] input, and z and m[3:0] output. Create and add Verilog modules to perform comparator_dataflow, lab2_circuitA_dataflow functionality using the dataflow constructs, instantiate mux_2to1 (of Lab 1) and connect them as shown in the above figure.

- 2-1-3. Add the provided testbench (lab2_2_1_partA_tb.v) to the project.
- 2-1-4. Simulate (behavioral simulation) the design for 200 ns and verify the design works.
- 2-1-5. Extend the design by creating the top-level module (lab2_2_1) to have bcdto7segment_dataflow decoder (that you developed in Lab 1) and provide one 7-bit output seg0 instead of m.
- 2-1-6. Add the appropriate board related master XDC file to the project and edit it to include the related pins. Assign v input to **SW3-SW0**, z to **LED0**, and seg0 to 7-segment display cathodes, **CA-CG**, and assign **an** to the pins **J17, J18, T9, J14, P14, T14, K2, U13** (for Nexys4 DDR) or **U2,U4,V4,W4** (for Basys3).
- 2-1-7. Synthesize and implement the design.
- 2-1-8. Generate the bitstream, download it into the Basys3 or the Nexys4 DDR board, and verify the functionality.
- 2-1-9. **Demonstrate simulation results, working circuit and Verilog code to the TA.**
- 2-2. **Model a 2-out-of-5 binary code and display a 4-bit binary coded decimal input number onto five LEDs. Use dataflow modeling.**
 - 2-2-1. Open Vivado and create a blank project called lab2_2_2.
 - 2-2-2. Create and add a hierarchical design with 4-bit input (x[3:0]) and 5-bit output(y[4:0]). Use dataflow modeling statements only.
 - 2-2-3. Add the appropriate board related master XDC file to the project and edit it to include the related pins. Assign **SW3 -SW0** to x and **LED4 to LED0** to y.
 - 2-2-4. Synthesize and implement the design.
 - 2-2-5. Generate the bitstream, download it into the Basys3 or the Nexys4 DDR board, and verify the functionality.
 - 2-2-6. **Demonstrate the working circuit and Verilog code to the TA.**

Performing Addition

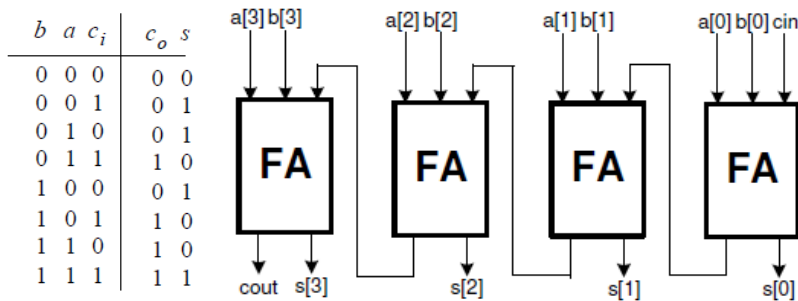Part 3

When two one-bit numbers are added, they may produce two bits output. For example, $1 + 1 = 10$ (all in binary). When you add three one-bit numbers the result will still be two bits, e.g. $1 + 1 + 1 = 11$. This simple operation can be viewed as adding two bits with carry in from the lower significant operation, resulting into sum and carry out- the left bit is carry out and the right bit is sum. The figure below shows a 4-bit adder. Since the carry is rippled from least significant bit position (cin) to the most significant position (cout), such adder is called ripple carry adder.




3-1. Create a 4-bit ripple carry adder using dataflow modeling.

- 3-1-1. Open Vivado and create a blank project called lab2_3_1.
- 3-1-2. Create and add the Verilog module named fulladder_dataflow with three inputs (a, b, cin) and two outputs (s and cout) using dataflow modeling. All inputs and outputs should be one-bit wide.
- 3-1-3. Add the provided testbench (fulladder_dataflow_tb.v) to the project.
- 3-1-4. Simulate the design for 80 ns and verify that the design works
- 3-1-5. Create and add the Verilog module (called rca_dataflow) to the project with three inputs (a, b, cin) and two outputs (cout and s) instantiating the full adder (FA) four times and connecting them as necessary. The a, b, and s should be a 4-bit vector and cin and cout should each be one-bit wide.
- 3-1-6. Add the appropriate board related master XDC file to the project and edit it to include the related pins. Assign a to **SW4-SW7**, b to **SW0-SW3**, s to **LED0-LED3**, cin to **SW15**, and cout to **LED15**.
- 3-1-7. Synthesize and implement the design.
- 3-1-8. Generate the bitstream, download it into the Basys3 or the Nexys4 DDR board, and verify the functionality.
- 3-1-9. **Demonstrate the working circuit and Verilog code to the TA.**

Improving Addition Speed

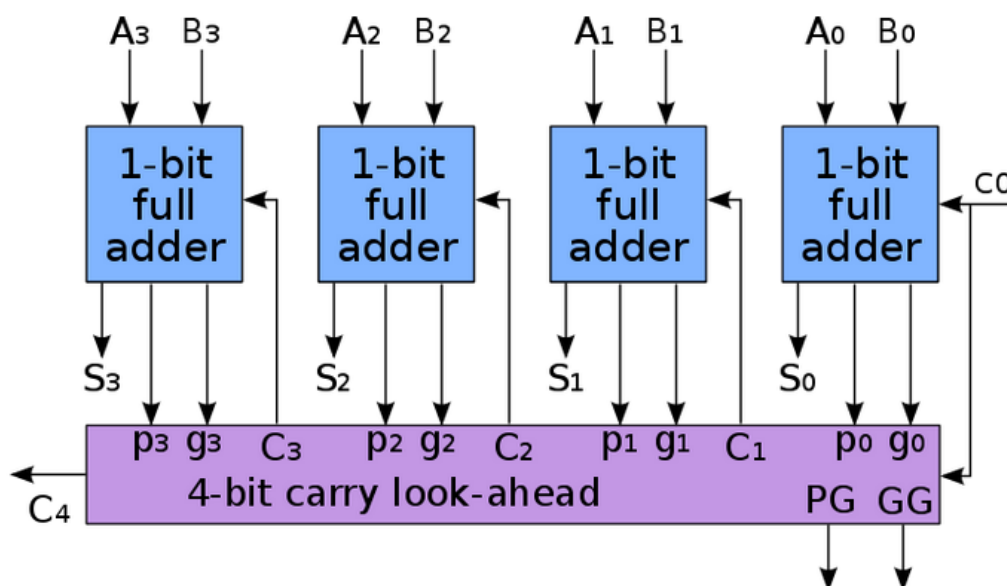Part 4

The ripple-carry adder takes a long time to compute when two large numbers (e.g. 8, 16, 32 bits) are added. To reduce the computation time, another structure called a carry look-ahead adder (see figure below) can be used. It works by creating two signals (P and G) for each bit position, based on whether a carry is propagated through a less significant bit position (at least one input is a '1'), generated in that bit position (both inputs are '1'), or killed in that bit position (both inputs are '0'). After P and G are generated, the carries for every bit position are created. This allows the circuit to “pre-process” the two numbers being added to determine the carry ahead of time. Then, when the actual addition is performed, there is no delay from waiting for the ripple-carry effect. Below is a simple 4-bit carry look-ahead circuit that combines with 4 ripple carry adders. The logic for the circuit can be seen below (Where $P_i = A_i + B_i$, $G_i = A_i \cdot B_i$ and $C_{i+1} = G_i + P_i \cdot C_i$). From the final equations you can see that all the carry bits can be calculated in parallel (i.e. individual carry bits only depend on C_0 and the generate and propagate bits). The penalty is that you have to add extra circuitry to speed up the calculation which will increase power consumption and silicon area/FPGA utilization.



$$C_1 = G_0 + P_0 \cdot C_0,$$

$$C_2 = G_1 + P_1 \cdot C_1,$$

$$C_3 = G_2 + P_2 \cdot C_2,$$

$$C_4 = G_3 + P_3 \cdot C_3.$$

Substituting C_1 into C_2 , then C_2 into C_3 , then C_3 into C_4 yields the expanded equations:

$$C_1 = G_0 + P_0 \cdot C_0,$$

$$C_2 = G_1 + G_0 \cdot P_1 + C_0 \cdot P_0 \cdot P_1,$$

$$C_3 = G_2 + G_1 \cdot P_2 + G_0 \cdot P_1 \cdot P_2 + C_0 \cdot P_0 \cdot P_1 \cdot P_2,$$

$$C_4 = G_3 + G_2 \cdot P_3 + G_1 \cdot P_2 \cdot P_3 + G_0 \cdot P_1 \cdot P_2 \cdot P_3 + C_0 \cdot P_0 \cdot P_1 \cdot P_2 \cdot P_3.$$

4-1. Create a carry look-ahead adder circuit by modifying the project of 3-1 and using dataflow modeling.

- 4-1-1. Open Vivado and open the project you had created in lab2_3_1 and save it as lab2_4_1.
- 4-1-2. Modify the project files of lab2_3_1 as necessary to perform the addition of two four-bit numbers using the carry look-ahead structure and outputting the result on the LEDs. Provide carry-in through SW15. Hint: You will need to modify FA to output P_i and G_i , and then create and add another module CLA to perform the carry look ahead function that takes c_0 , p_i and g_i ($i=0$ to 3) and outputs c_{i+1} .
- 4-1-3. Modify the XDC file to provide input b through **SW3-SW0**, a through **SW7-SW4**, cin as **SW15**. Output cout through **LED15** and sum through **LED3-LED0**.
- 4-1-4. Synthesize and implement the design.
- 4-1-5. Generate the bitstream, download it into the Basys3 or the Nexys4 DDR board, and verify the functionality.
- 4-1-6. **Demonstrate the working circuit and Verilog code to the TA.**

Conclusion

In this lab, you learned how to define numbers in various radix systems. You also designed various number conversion circuits using dataflow modeling. You also learned a technique of improving addition speed.